

## The Perfect Circuit

The perfect circuit is overunity (more reactant output than energetic input), staccato wedges of self-regulating amplitudes of current and voltage surges<sup>1 2</sup> maintaining a consistent level of output, and is simple to conceive and is buildable. Eric Dollard's analog computer in LMD mode<sup>3</sup> (longitudinal magneto-dielectric) laid on top of a dielectrical canister of helium fulfills these requirements providing a slight negative parallel resistance of  $-10\text{m}\Omega$  among its four capacitors, C1 through C4, in addition to their  $+100\text{m}\Omega$  of equivalent series resistance. The input is a fractional sine wave of 13kHz and  $1\mu\text{V}$  quickly cutoff after one femto second of duration so as to prevent the suppression of reactance within the body of this circuit. This constitutes a “perpetual motion machine”<sup>4</sup> after this initial input is disregarded! This is also a perpetual motion machine of the first kind in as much as the law of Lenz has been defeated. In other words, there is no back EMF in the coils to contribute to any delay among the capacitors which are all charging and discharging at exactly the same time (without any time delay)<sup>5</sup> as if there were no speed of light and all because of impedance matching.<sup>6</sup>

The eight resistors, R2 through R9, of  $1.1\text{k}\Omega$  may be increased to  $4\text{k}\Omega$  to quickly shut down this circuit if – in addition to these eight resistors, another two resistors of  $4\text{k}\Omega$  are each placed inline with the two inductors, L1 & L2.

Not only do the neon bulbs periodically arc to collapse the overunity escalation towards infinity to prevent this circuit from exploding into its self-destruction, but the current and the voltage components of the triangular output waveforms are totally in phase with each other with zero degrees of separation between them and are oscillating at approximately 50–75kHz (more or less) after an initial warm up period of less than 150 milli seconds! The input current at the sine wave generator, V1, gives a short burst of  $1.22\text{e}-29$  amps at startup and then quickly drops to zero amps at 770.6 nano seconds and remains there for the remainder of the simulation. The input voltage is a steady sine wave of 13kHz, but this does not pass through the switch, SW1, after the switch closes upon reaching one femto second after start up.

When applying a reduction of negative parallel resistance (of  $-10$  milli Ohms as compared with  $-100$  milli Ohms for example) within all four capacitors, C1 through C4, their capacitances must be reduced and the inductances of the shunt transformers, K1 through K3, must also be reduced or else this circuit will blow up for failure of the spark gaps to fire rapidly enough to keep up with the accelerated growth of electrical amplitude! Their capacitive and inductive amplitudes are directly related to this circuit's output. In other words, the greater their capacitances and/or inductances, then the greater will be the output generally speaking.

---

1 [Second Order Constant Coefficient Linear Equations | Differential Equations | Mathematics | MIT OpenCourseWare](#)

2 [Poles and Vibrations](#)

3 [Eric Dollard's Analog Computer as a Power Amplifier](#) on Quora

4 [Ben Fitzgearl's answer to What would happen if an induced current did not oppose the change that caused it, as in Lenz's law?](#) on Quora

5 [Eric Dollard - Origin of Energy Synthesis](#) – 3 hr, 45 min, 15 sec into this YouTube video

6 [Impedance of Same Magnitude](#) on Quora

Micro-Cap 12.2.0.3 (32 bit) - [C:\Documents and Settings\Dell User\My Documents\TEXTS\Energy\Epub\Falstad\analog-computer-v10a-ON.CIR]

File Edit Component Windows Options Analysis Design Model Help

Put a set of switches - in each location where there is a 1.1 kilo Ohm resistor - to add another 2.9 kilo Ohms of resistance to bring the total resistance to 4 kilo Ohms. Plus, add an additional pair of resistors of 4 kilo Ohms, each, inline with the inductive loads, L1 & L2. This will make it possible to turn this circuit OFF.

<https://is.gd/analogcomputer> switch parameters: duration & resistances » T,0,1e-15,1e-9,1e50

1fs burst of a 1 $\mu$ V sine wave at 13kHz.

Two daisy-chained modules of Eric Dollard's LMD analog computer (longitudinal magneto-dielectric).

This circuit could be laid on top of a dielectrical canister of helium for improved performance and reduction of mass?

Notice that this is overunity and this is \*real power\*, not reactive power, since the voltage and current triangular waves are in sync (which is obvious during any window of a few hundred micro seconds of their career) with zero degrees phase difference between them.

What we have, here, is the replication of the utility grid scaled down to a neighborhood power unit. The shunt inductances and the resistors represent the magnetizability of a transmission line along with the resistance of its length. Capacitors, especially C5 and C6, have the greatest units of amperage elevated by a factor ten units over their units of voltage.

All six capacitors have +100 milli Ohms of equivalent series resistance. Capacitors, C1 through C4, have -10 milli Ohms of equivalent parallel resistance. C5 & C6, stabilize the output. Inductors, L1 & L2, have 1 Ohm of series resistance and 1 $\mu$  Farad of parallel capacitance.

analog-computer-v10a-ON.CIR analog-computer-v10b-OFF.CIR

Select Mode

Micro-Cap 12.2.0.3 (32 bit) - [C:\Documents and Settings\Dell User\My Documents\TEXTS\Energy\Epub\Falstad\analog-computer-v10a-ON.CIR]

File Edit Component Windows Options Analysis Design Model Help

Put a set of switches - in each location where there is a 1.1 kilo Ohm resistor - to add another 2.9 kilo Ohms of resistance to bring the total resistance to 4 kilo Ohms. Plus, add an additional pair of resistors of 4 kilo Ohms, each, inline with the inductive loads, L1 & L2. This will make it possible to turn this circuit OFF.

<https://is.gd/analogcomputer> switch parameters: duration & resistances » T,0,1e-15,1e-9,1e50

1fs burst of a 1 $\mu$ V sine wave at 13kHz.

Two daisy-chained modules of Eric Dollard's LMD analog computer (longitudinal magneto-dielectric).

This circuit could be laid on top of a dielectrical canister of helium for improved performance and reduction of mass?

Notice that this is overunity and this is \*real power\*, not reactive power, since the voltage and current triangular waves are in sync (which is obvious during any window of a few hundred micro seconds of their career) with zero degrees phase difference between them.



What we have, here, is the replication of the utility grid scaled down to a neighborhood power unit. The shunt inductances and the resistors represent the magnetizability of a transmission line along with the resistance of its length. Capacitors, especially C5 and C6, have the greatest units of amperage elevated by a factor ten units over their units of voltage.


All six capacitors have +100 milli Ohms of equivalent series resistance. Capacitors, C1 through C4, have -10 milli Ohms of equivalent parallel resistance. C5 & C6, stabilize the output. Inductors, L1 & L2, have 1 Ohm of series resistance and 1 $\mu$  Farad of parallel capacitance.



analog-computer-v9b-OFF.CIR analog-computer-v10a-ON.CIR



Select Mode





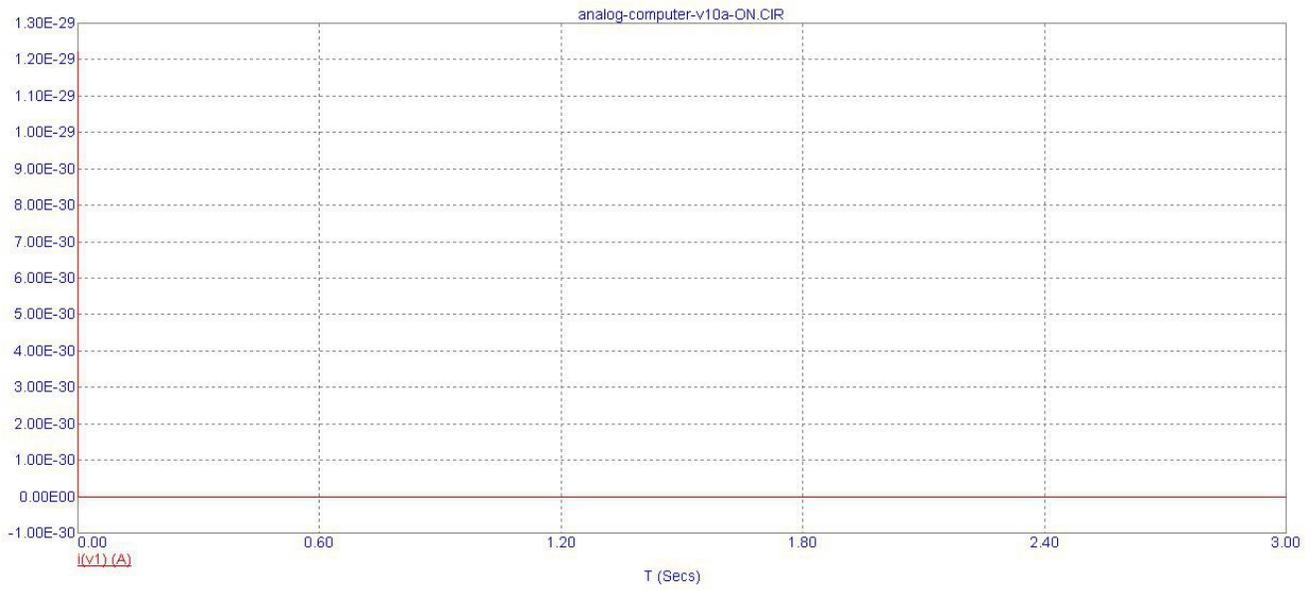
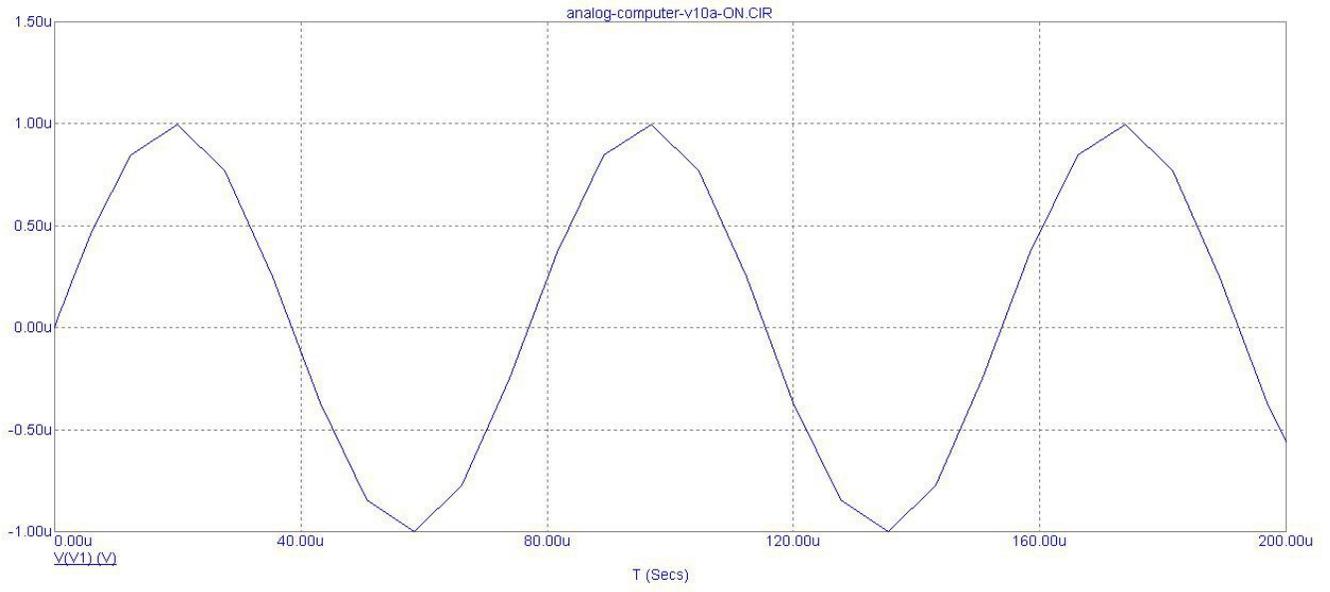



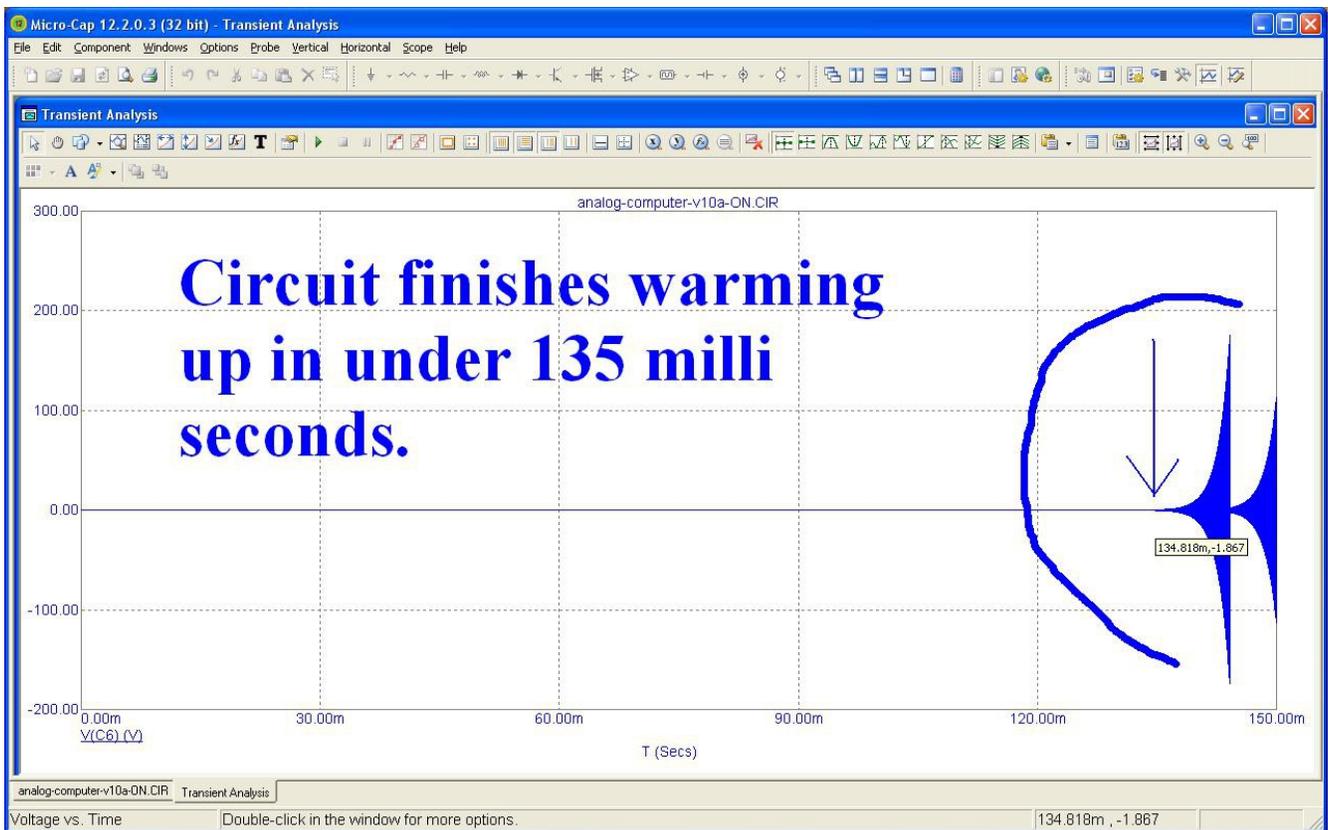


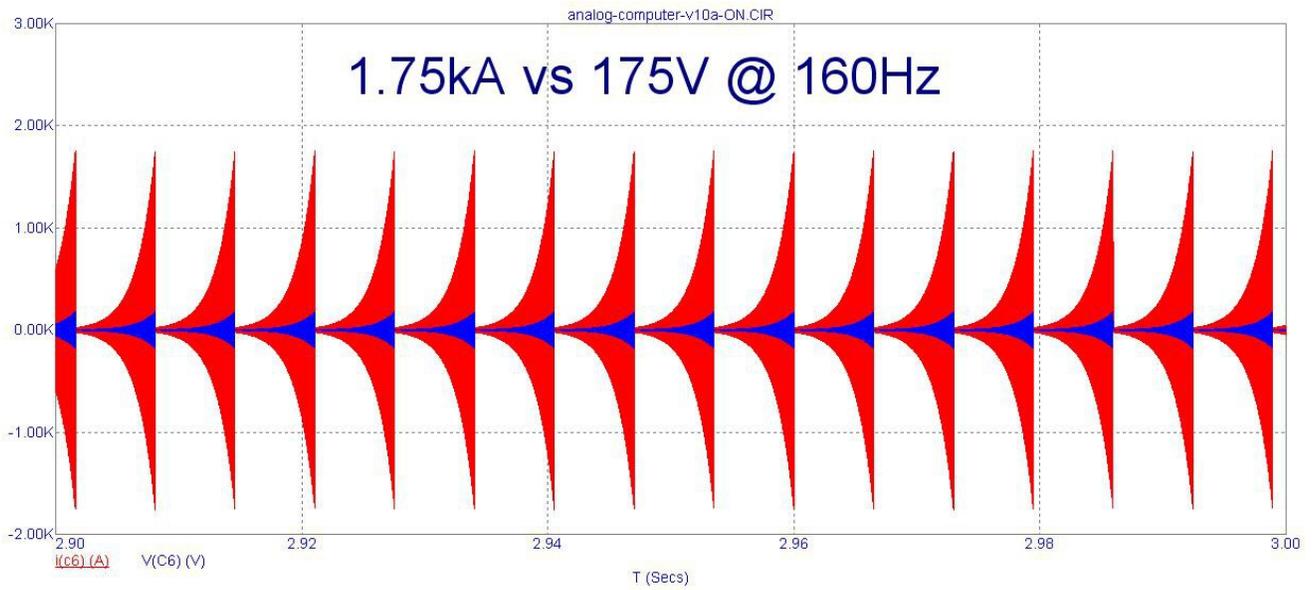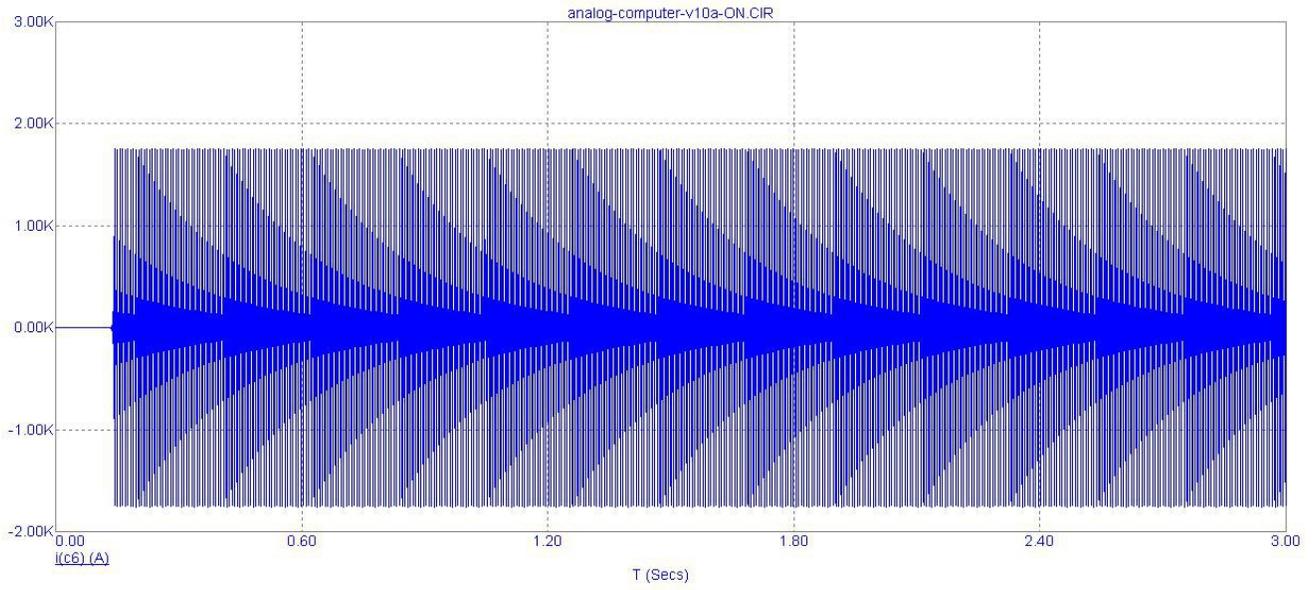


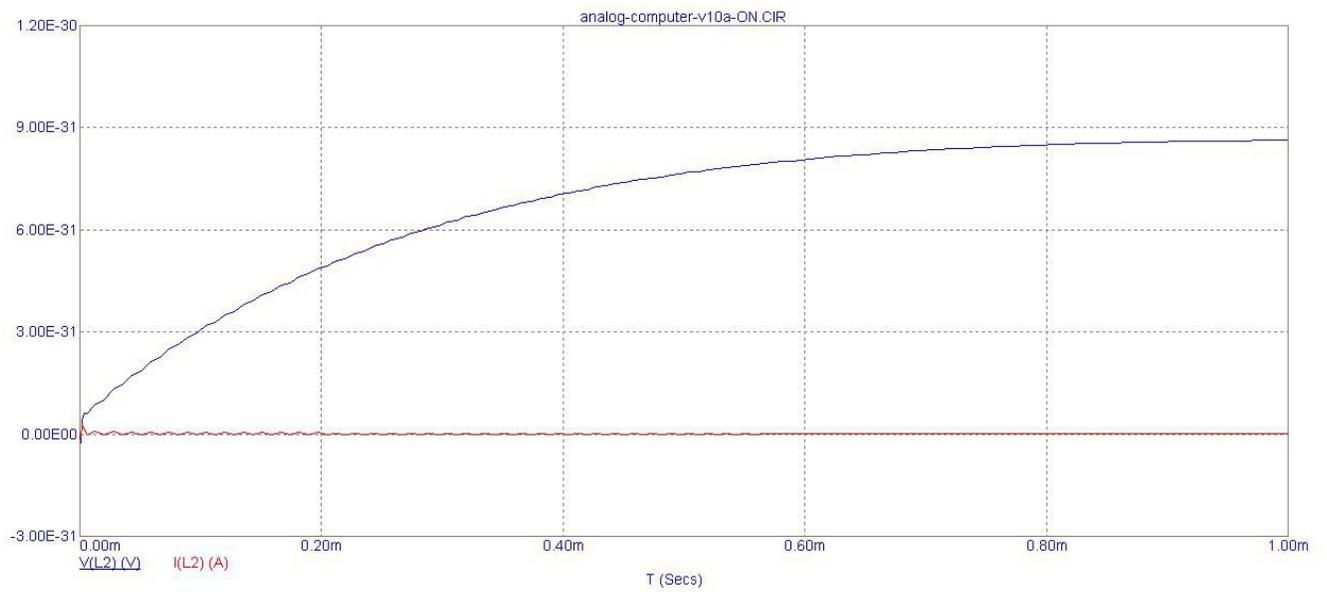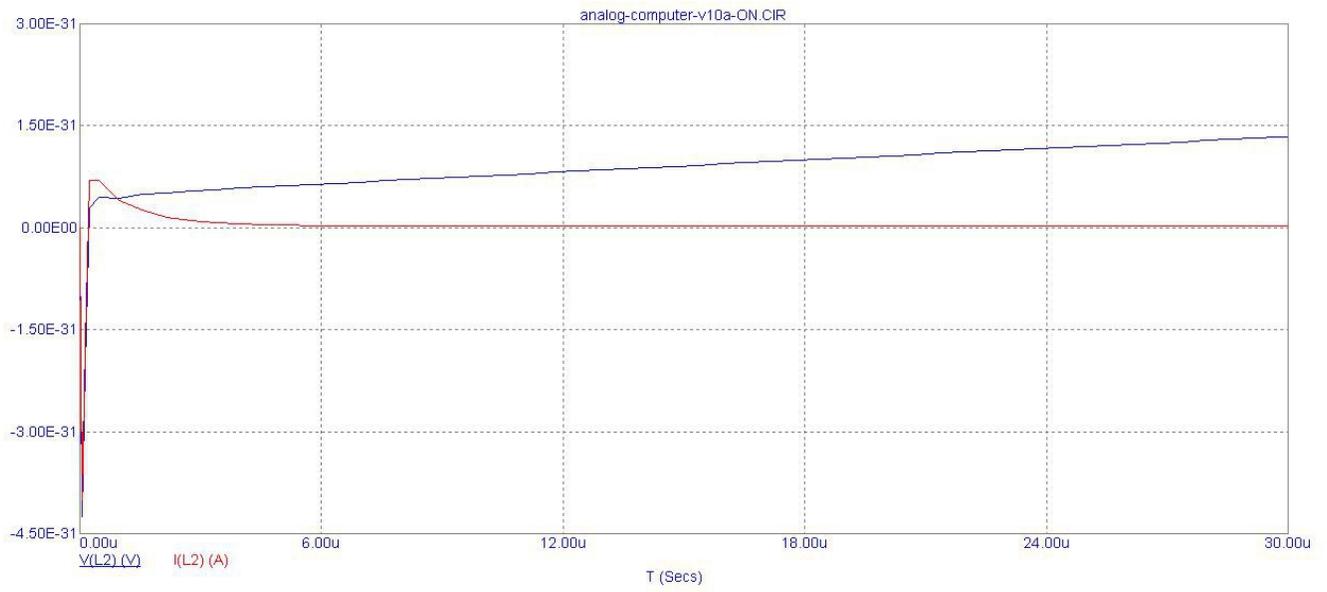

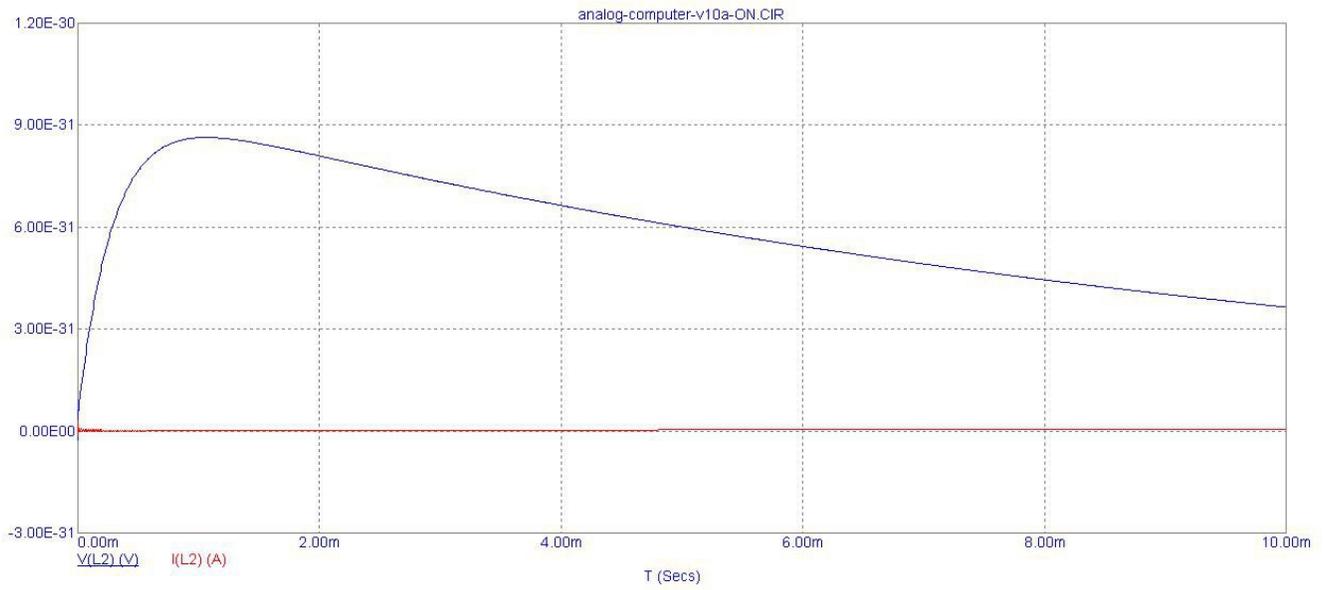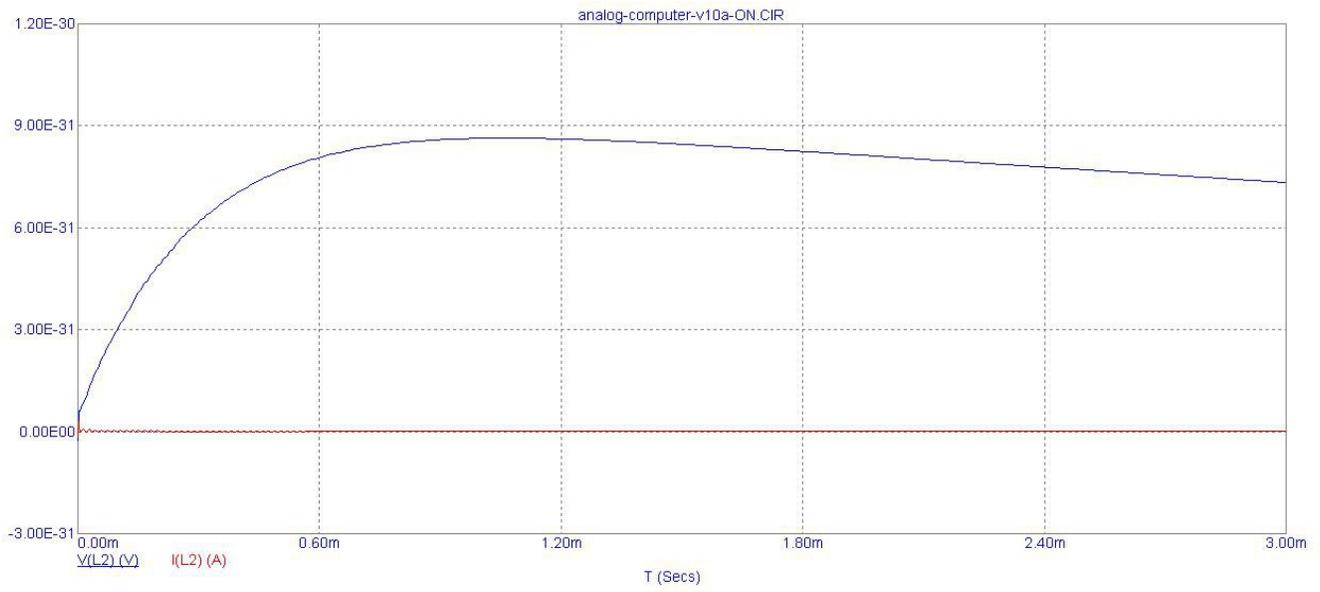

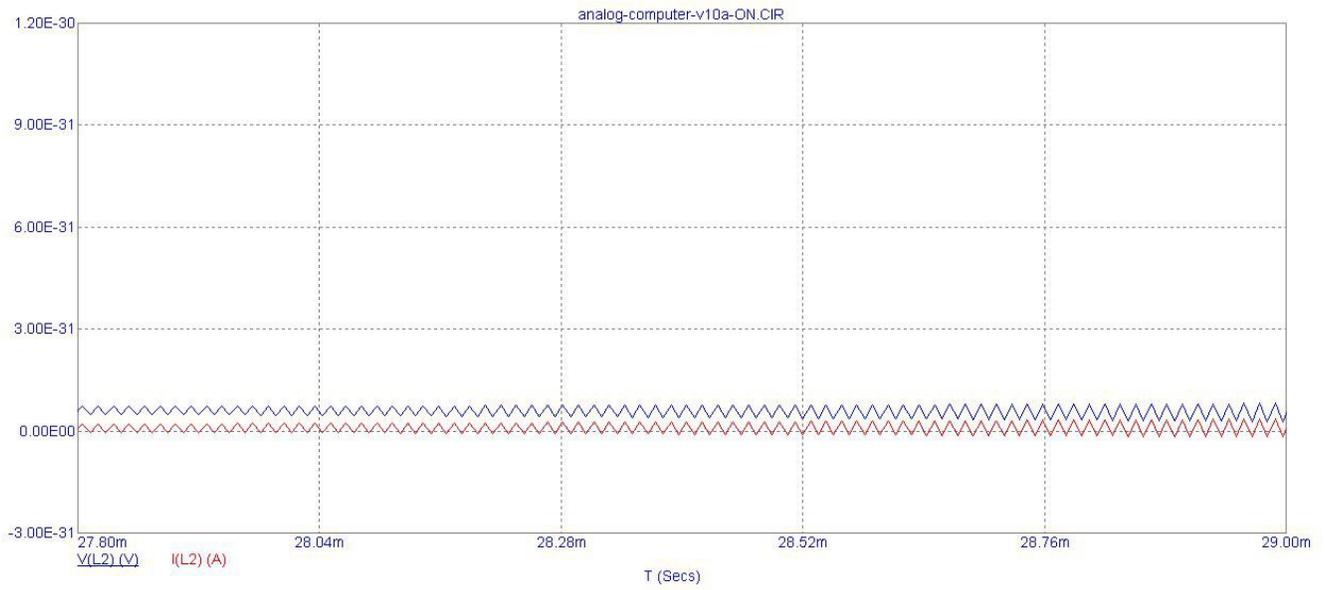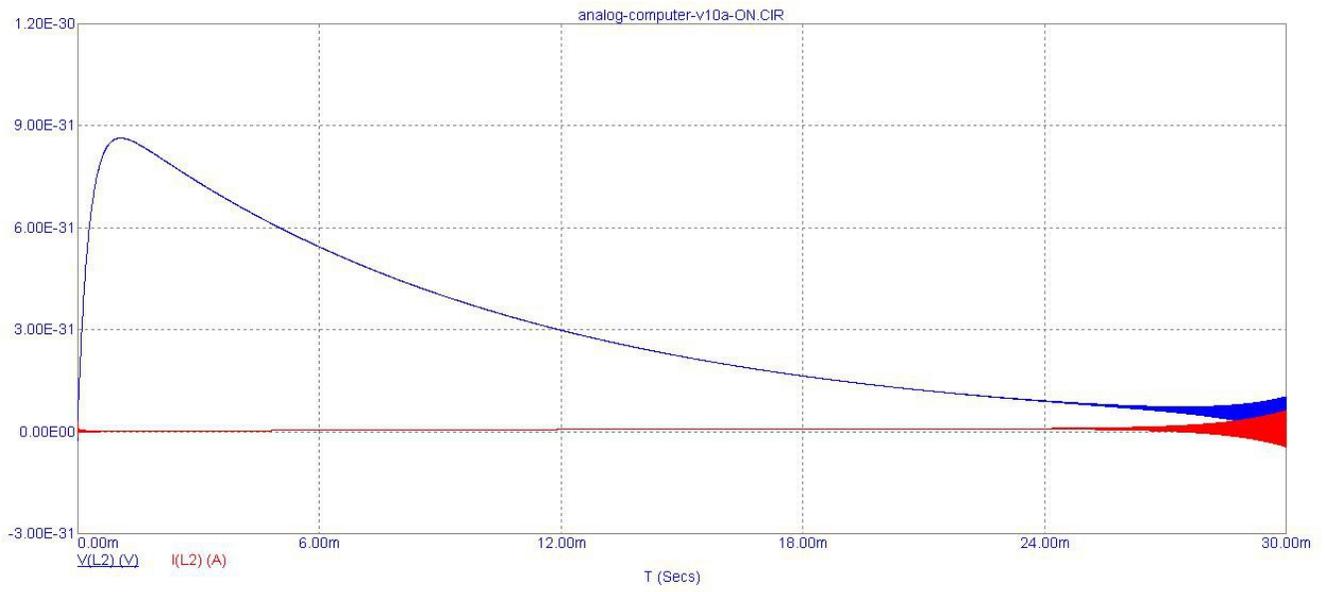

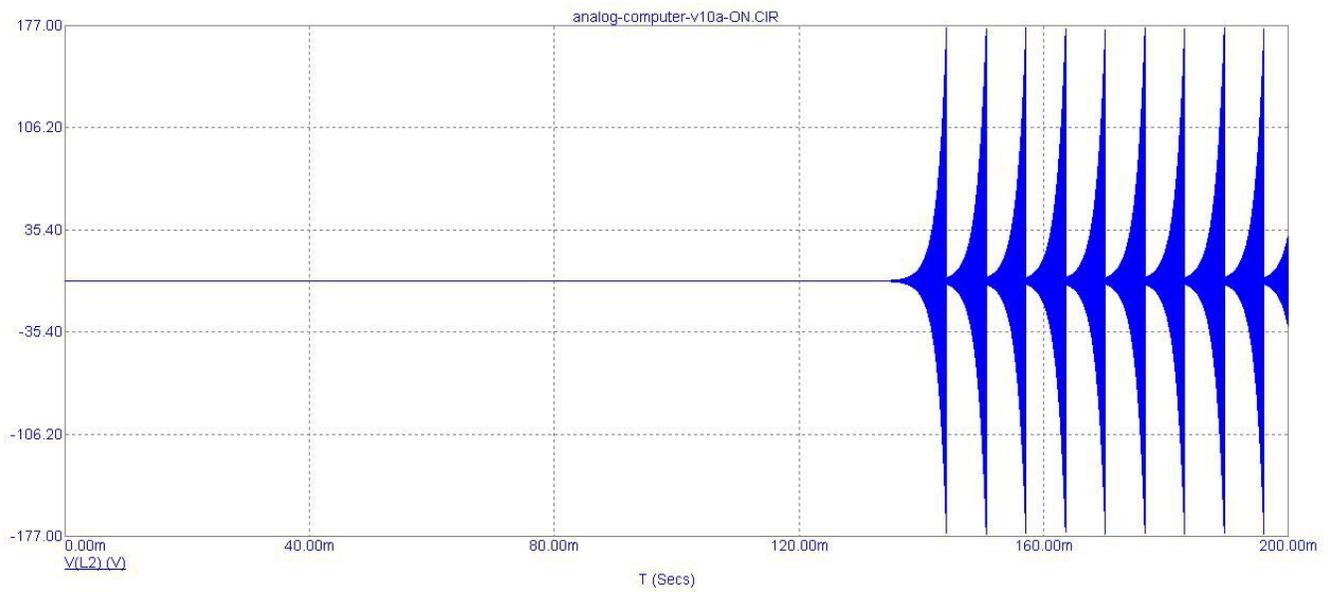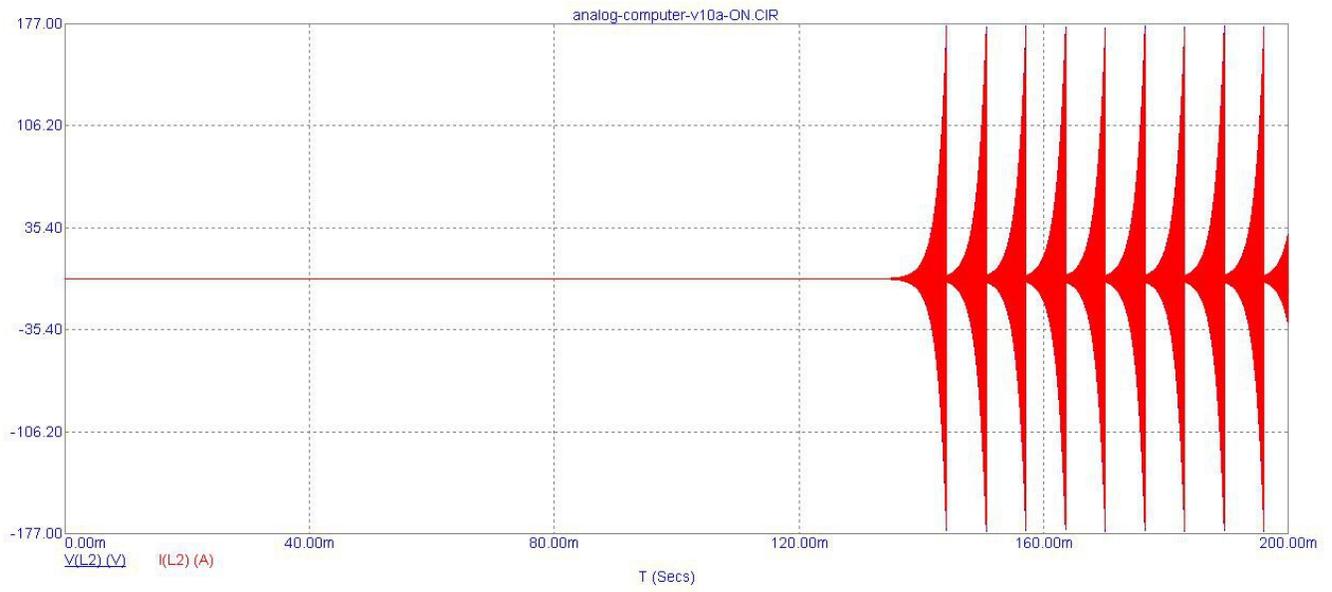

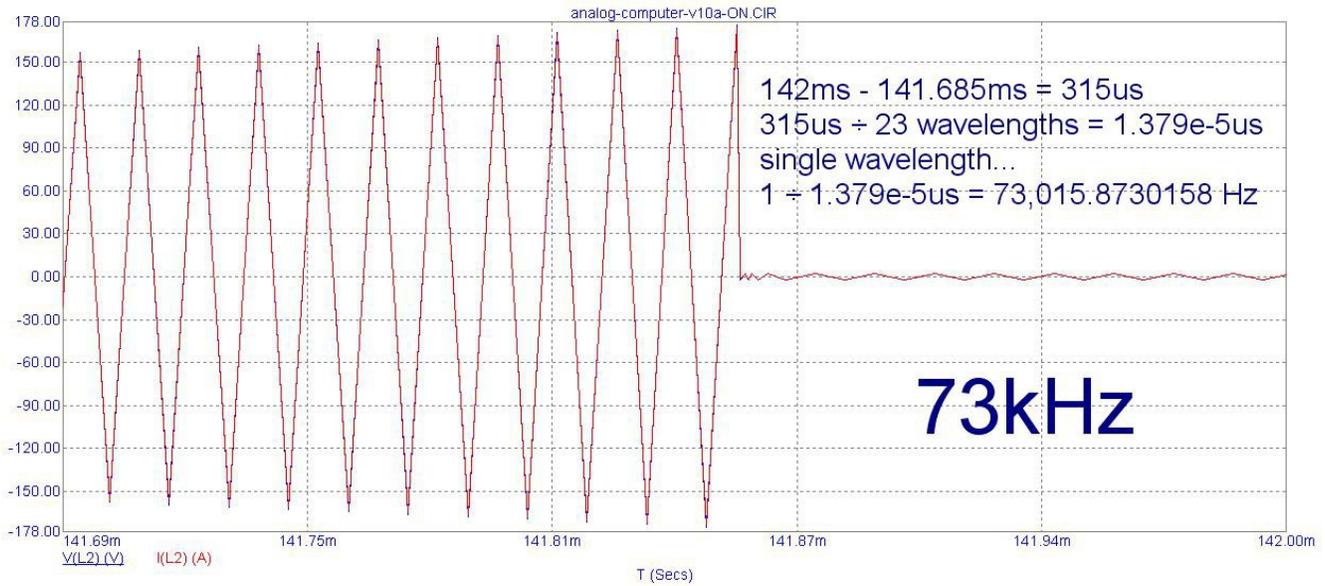

Micro-Cap 12.2.0.3 (32 bit) - [C:\Documents and Settings\Dell User\My Documents\TEXTS\Energy\Epub\Falstad\analog-computer-v10b-OFF.CIR]

File Edit Component Windows Options Analysis Design Model Help

Put a set of switches - in each location where there is a 1.1 kilo Ohm resistor - to add another 2.9 kilo Ohms of resistance to bring the total resistance to 4 kilo Ohms. Plus, add an additional pair of resistors of 4 kilo Ohms, each, inline with the inductive loads, L1 & L2. This will make it possible to turn this circuit OFF.

<https://is.gd/analogcomputer> switch parameters: duration & resistances » T,0,1e-15,1e-9,1e50

1fs burst of a 1μV sine wave at 13kHz.

Two daisy-chained modules of Eric Dollard's LMD analog computer (longitudinal magneto-dielectric).

This circuit could be laid on top of a dielectrical canister of helium for improved performance and reduction of mass?

Notice that this is overunity and this is \*real power\*, not reactive power, since the voltage and current triangular waves are in sync (which is obvious during any window of a few hundred micro seconds of their career) with zero degrees phase difference between them.

What we have, here, is the replication of the utility grid scaled down to a neighborhood power unit. The shunt inductances and the resistors represent the magnetizability of a transmission line along with the resistance of its length. Capacitors, especially C5 and C6, have the greatest units of amperage elevated by a factor ten units over their units of voltage.

All six capacitors have +100 milli Ohms of equivalent series resistance. Capacitors, C1 through C4, have -10 milli Ohms of equivalent parallel resistance. C5 & C6, stabilize the output. Inductors, L1 & L2, have 1 Ohm of series resistance and 1μ Farad of parallel capacitance.

analog-computer-v10b-OFF.CIR

Select Mode

Micro-Cap 12.2.0.3 (32 bit) - [C:\Documents and Settings\Dell User\My Documents\TEXTS\Energy\Pub\Falstad\analog-computer-v10b-OFF.CIR]

File Edit Component Windows Options Analysis Design Model Help

Put a set of switches - in each location where there is a 1.1 kilo Ohm resistor - to add another 2.9 kilo Ohms of resistance to bring the total resistance to 4 kilo Ohms. Plus, add an additional pair of resistors of 4 kilo Ohms, each, inline with the inductive loads, L1 & L2. This will make it possible to turn this circuit OFF.

<https://is.gd/analogcomputer> switch parameters: duration & resistances » T,0,1e-15,1e-9,1e50

1fs burst of a 1μV sine wave at 13kHz.

Two daisy-chained modules of Eric Dollard's LMD analog computer (longitudinal magneto-dielectric).

This circuit could be laid out on top of a dielectrical canister of helium for improved performance and reduction of mass?


Notice that this is overunity and this is \*real power\*, not reactive power, since the voltage and current triangular waves are in sync (which is obvious during any window of a few hundred micro seconds of their career) with zero degrees phase difference between them.

What we have, here, is the replication of the utility grid scaled down to a neighborhood power unit. The shunt inductances and the resistors represent the magnetizability of a transmission line along with the resistance of its length. Capacitors, especially C5 and C6, have the greatest units of amperage elevated by a factor ten units over their units of voltage.

All six capacitors have +100 milli Ohms of equivalent series resistance. Capacitors, C1 through C4, have -10 milli Ohms of equivalent parallel resistance. C5 & C6, stabilize the output. Inductors, L1 & L2, have 1 Ohm of series resistance and 1μ Farad of parallel capacitance.

analog-computer-v9b-OFF.CIR analog-computer-v10b-OFF.CIR

Select Mode

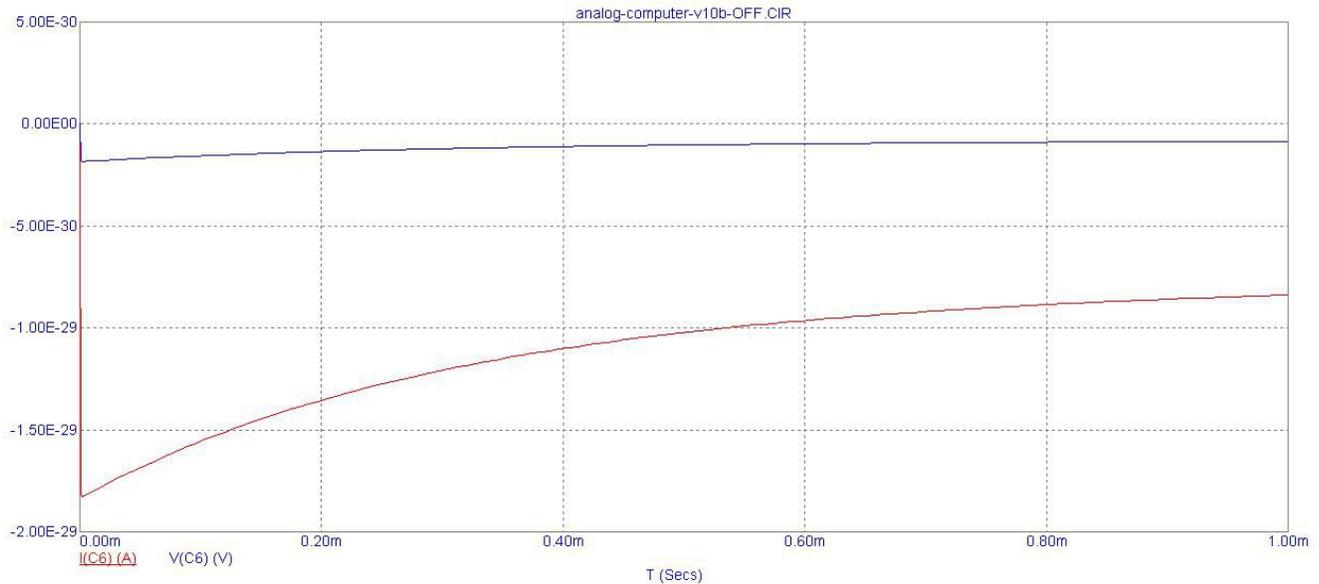

From an analysis of these virtual oscilloscope tracings, it becomes apparent (with a little forethought) that any load – dynamic or otherwise – applied to the circuit, from outside itself, will collapse it's overunity just as its spark gaps do this (periodically) causing the unique staccato wedge-shaped surges pulsing 160 times a second (10th image) – more or less.

But take heart! That does not mean this is a worthless demonstration of profligate power.


All we have to do is figure out the right instance in which to apply this. Isn't that what was said of many inventions that they couldn't imagine what it may be good for?

Well, imagine if you will, a situation in which you were *not* trying to energize something solid and material, but (instead) are attempting to energize the space surrounding a circuit.

This is precisely the situation of a UFO – or, what Nikola Tesla called his “Ideal Flying Machine” (without wings, propellers, or propellant) according to William Lyne's text, “Occult Ether Physics”.<sup>7 8 9</sup>  
10 11 12

Despite this hypothetical concern, if it *is* possible to put these triangle waves to good use powering a motor, then pulse width modulation may be useful for interfacing these triangular waves with whatever application is required, such as an EV (my dream car).<sup>13 14</sup> [Thanks goes to Roger Larson for this insight.]<sup>15</sup>

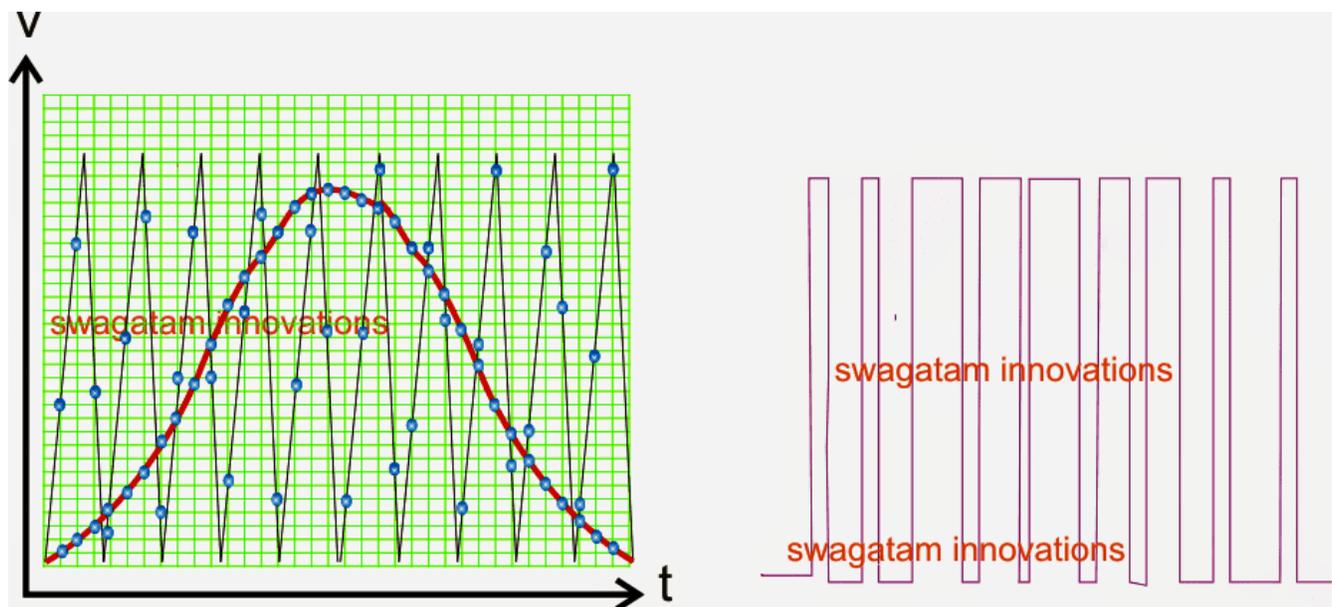***The signal with the higher frequency is termed as the carrier signal,  
while the slower sample signal is called the modulating input.***



7 [Occult ether physics William Lyne at DuckDuckGo](#)

8 [US10144532B2 - Craft using an inertial mass reduction device - Google Patents](#)

9 [Moment of Inertia](#)

10 [Pentagon aliens William Lyne at DuckDuckGo](#)

11 [The Inventions Researches and Writings of Nikola Tesla : Thomas Commerford Martin : Free Download, Borrow, and Streaming : Internet Archive](#)

12 [Franco Bruno Corteletti's answer to What hard evidence suggests that gravity occurs among non-celestial and non-atomic objects such as between two bowling balls sitting on a wooden table or hung from two ropes? I am not convinced.](#)

13 [Pulse-width modulation - Wikipedia](#)

14 [Sine Pulse Width Modulation \(SPWM\) using Simulink](#)

15 [Roger Larson's answer to To what electrical uses may triangular waves be put?](#)

*“Electronic power devices when forced to operate with sinusoidal waves produce inefficient results since the devices tend to get relatively more hot compared to when operated with square wave pulses.*

*So the next best option for implementing a sine wave from an inverter<sup>16</sup> is by the way of PWM, which stands for Pulse width modulation.*

*PWM is an advanced way (digital variant) of putting forth an exponential waveform through a proportionately varying square pulse widths whose net value is calculated to exactly match the net value of a selected exponential waveform, here "net" value refers to the RMS value. Therefore a perfectly calculated PWM with reference to a given sine wave can be used as a perfect equivalent for replicating the given sinewave.”<sup>17</sup>*



*“The fewer times that a wave cycles, the less certain its frequency is. Taking this concept to its logical extreme, a short pulse—a waveform that doesn’t even complete a cycle—actually has no frequency, but rather acts as an infinite range of frequencies. This principle is common to all wave-based phenomena, not just AC voltages and currents.”<sup>18</sup>*

I find this intriguing regarding my so-called perfect circuit (above) since it’s input is an extreme fraction of one entire sine wave cycle (one femto second =  $1e-15$  seconds) for its 13kHz (76.9 micro second wave length) input. This fractional input is a 76.9 billion times shorter duration than the 13kHz sine wave length being inputted due to the very fast virtual switch, SW1 (in the circuit, above), cutting off the input shortly after it begins!

### ***For further reading (in no particular order)...***

- [Electronic Speed Controllers, page 1 of 10](#)
- [Automatic Inverter Output Voltage Correction Circuit](#)
- [Calculating Inductors in Buck Boost Converters](#)
- [Comparator Circuits using IC 741, IC 311, IC 339](#)
- [IC 555 Pinouts, Astable, Monostable, Bistable Circuits with Formulas Explored](#)
- [Inverter Voltage Drop Issue – How to Solve](#)
- [Scalar \(V/f\) Control of 3-Phase Induction Motors](#)
- [Constant Torque Motor Speed Controller Circuit](#)
- [How to Generate PWM Using IC 555 \(2 Methods Explored\)](#)
- [Understanding Scalar \(V/f\) Control for Induction Motors](#)
- [7 Modified Sine Wave Inverter Circuits Explored – 100W to 3kVA](#)
- [High Current Sensorless BLDC Motor Controller using Back EMF](#)

---

<sup>16</sup> [How to Build a 100 Watt, Pure Sine Wave Inverter](#)

<sup>17</sup> [Sine wave PWM \(SPWM\) Circuit using Opamp | Homemade Circuit Projects](#)

<sup>18</sup> [Square Wave Signals | Mixed-Frequency AC Signals | Electronics Textbook](#)