

THE SHORT DESCRIPTION OF HOW I MAKE FREE ENERGY – I take a step up / step down transformer and I feed it an Alternating Current and reverse its polarity of voltage with respect to the current. Hence, instead of current traveling from an area of voltage which is higher than its destination, I've managed to fool the current into traveling from an area of voltage which is non-existent towards an area of moderately high voltage. Since current moves voltage from one place to another, this results in the area of high voltage amassing more voltage. Also, due to feedback across the step-down transformer, this elevated voltage translates into an increase of current where the current is coming from at the expense of a little bit of the moderately high voltage. So, both sides magnify their amplitude. The net result is more power. But this power is not real; it is reactant power due to the total reversal of voltage polarity (which is a negative power factor of 180 degrees of separation between voltage and current. But no worries, for power factor correction from a simple resistor, such as: a spark gap (in the form of a neon bulb or fluorescent tube minus its ballast), or an arc lamp, or a battery, or a plain resistor, can easily and readily convert this reactant power into real power which our appliances can use. All of this is the result of mere stimulation of the circuit with a moderate to high frequency carried upon the back of a sine wave whose voltage is no more than 3 volts and no less than one micro volt. This lower limit is similar to what crystal radio sets dating from the 1920s used to run on powered such as they were from their aerial, alone – which was a short piece of wire no more than a few feet long. How's that for freedom from want!?