

# SPICE Analog Behavioral Modeling of Variable Passives

By **Christophe Basso**, Application Manager,  
ON Semiconductor, Toulouse, France

**I**n part one of this article (see “SPICE Analog Behavioral Modeling of Variable Passives,” March 2005, *Power Electronics Technology*), a method for modeling a variable resistor within SPICE was described. Here in part two, a similar technique is applied to model variable capacitors.


As we did in the previous article with the resistor, a capacitor can be portrayed by a voltage source obeying the following law:

$$V_c(t) = \frac{1}{C} \cdot \int I_c(t) \cdot dt$$


In other words, if we integrate the current flowing into our equivalent subcircuit capacitor and multiply it by the inverse of a control voltage  $V$ , we obtain a capacitor of value  $C = V$ . Unfortunately, there is no integral primitive in SPICE

since it involves the variable  $t$ , which is continuously varying. Therefore, why not capitalize on the equation and force the subcircuit current into a 1-F capacitor? By observing the resulting voltage over this 1-F capacitor, we have integrated  $I_c(t)$ .


**Fig. 1** shows how

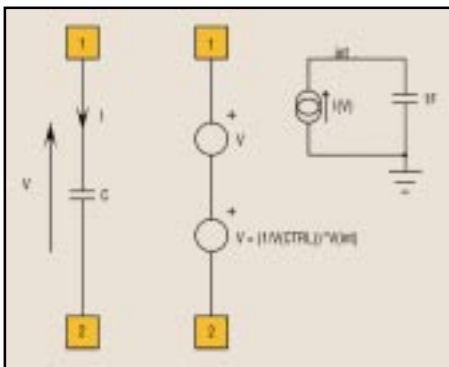

**Fig. 1.** Forcing a current into a 1-F capacitor produces the integration of a time-varying function in Spice.

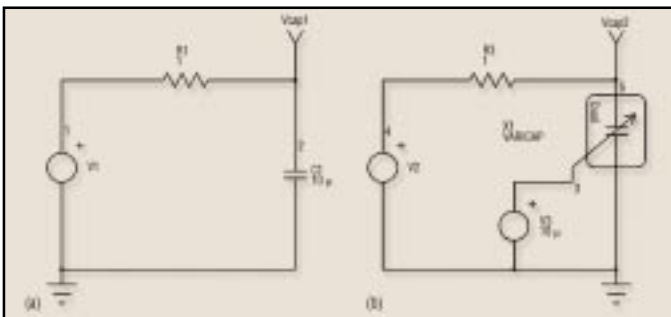

**Fig. 2.** In a real test circuit, a square wave source pulses a 10- $\mu$ F capacitor (a). This same circuit is then modeled in Spice (b).

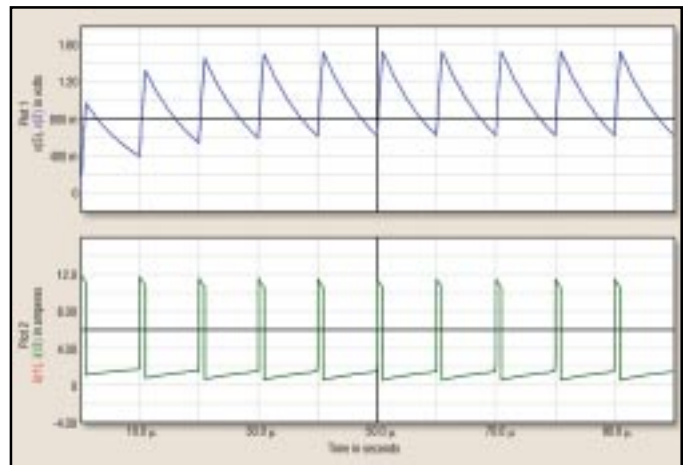

**Fig. 3.** The variable and the classical capacitor models produce similar waveforms, as shown in these plots of voltages and currents obtained from both the real capacitor and the variable one modeled in Spice.

we can build the subcircuit.

In **Fig. 1**, the dummy source  $V$  routes the current into the 1-F capacitor, which develops the integrated voltage on the “int” node. Then, once multiplied by the inverse of the CTRL node voltage, it mimics our variable capacitor. **Fig. 2** shows an actual test circuit used to verify the validity of our Spice model. **Fig. 3** displays voltages and currents obtained from both the real capacitor and the variable one modelled in Spice. There is no difference between plots.

Below are the models in both IsSpice and PSpice:

**IsSpice**

```
.SUBCKT VARICAP 1 2 CTRL
R1 1 3 1u
VC 3 4
BC 4 2 V=(1/v(ctrl))*v(int)
BINT 0 INT I=I(VC)
CINT INT 0 1
.ENDS
```

**PSpice**

```
.SUBCKT VARICAP 1 2 CTRL
R1 1 3 1u
VC 3 4
EC 4 2 Value = { (1/v(ctrl))*v(int) }
GINT 0 INT Value = { I(VC) }
CINT INT 0 1
.ENDS
```

Tests also were run in ac analysis where the model confirmed its accuracy in the frequency domain. **PETech**