



[▶ Watch now](#)

## Attempting to build a Pseudo-Replica of an LTSpice Simulation

(linked below)




VINYASI

JUL 05, 2026

# Infinite Instantaneous Power from an LTSpice Simulation of a Neon Core Transformer.

VINYASI · JUL 4

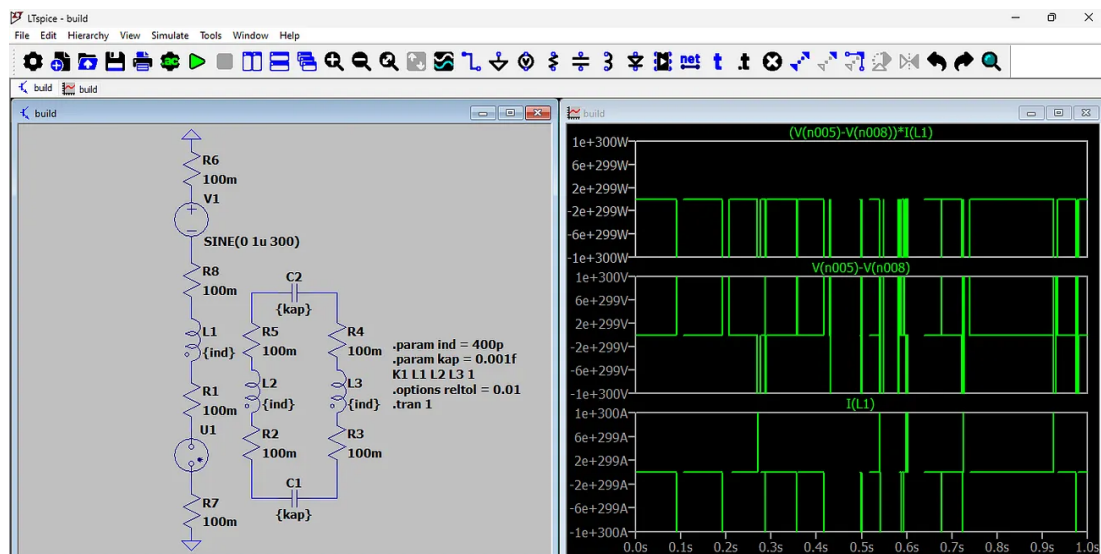

Netlist:

[Read full story](#)

I didn't do a very good job since my capacitors are way too large. I used 330 nano Farads while the simulation, above, uses one thousand times smaller than a femto Farad (which is a million times smaller than a pico Farad). Oops!

But it was fun building something for a change! ;-)